

❖ Chapter 2: Combinational Logic/Combinational Circuits


Lecture Practice due Apr 8, 2023 10:37 PDT Completed


Combinational Circuits

1/1 point (graded)


[Keyboard Help](#)

 Drag the circuits into the boxes to classify them as combinational or non combinational.





**Combinational
Circuit**

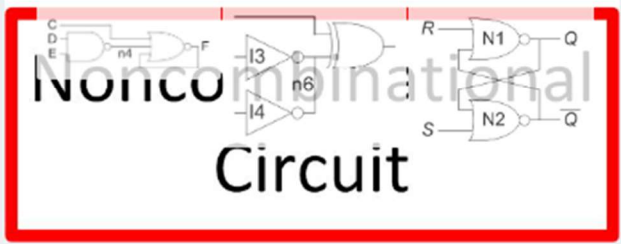

**Noncombinational
Circuit**

 Reset

FEEDBACK

Good work! You have distinguished combinational circuits.

Consider the following truth table.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Sum of Products

1/1 point (graded)

Give a sum of products expression for the truth table above. Read $\sim A$ as NOT(A) (like A with a bar over the top).

☐ $Y = A$

☒ $Y = (\sim A)(\sim B) + AB$

☐ $Y = (\sim A)B + A(\sim B)$

☐ $Y = \sim(A \wedge B)$



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Duality

1/1 point (graded)

What is the dual of $0 * 0 = 0$?

☐ $0 + 0 = 0$

☒ $1 + 1 = 1$

☐ $1 * 1 = 1$



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Duality

1/1 point (graded)

Let $(\sim X)$ mean NOT X. Propose a "Super Involution" Theorem: $(\sim(\sim(\sim B))) =$

☐ 0

☐ 1

☐ B

☒ $(\sim B)$



Submit

Try again (1 attempt remaining)

Show answer

XOR Identity

1/1 point (graded)

The identity element I for XOR such that $B \text{ XOR } I = B$ is:

☒ 0

☐ 1

☐ There is no identity element for XOR



Submit

Try again (1 attempt remaining)

Show answer

XOR Null Element

1/1 point (graded)

The null element N for XOR such that $B \text{ XOR } N = N$ is:

☐ 0

☐ 1

☒ There is no null element for XOR



Submit

Try again (1 attempt remaining)

Show answer

Theorems

1/1 point (graded)

The theorem that $X+Y = Y+X$ is known as:

☐ Associativity

☐ Distributivity

☒ Commutativity



Submit

Try again (1 attempt remaining)

Show answer

Duality

1/1 point (graded)

What is the dual of the covering theorem $B*(B+C) = B$?

☐ $B + C = C + B$

☐ $(C+B)*B = B$

☒ $B+(B*C)=B$



Submit

Try again (1 attempt remaining)

Show answer

Proof

1/1 point (graded)

How can you prove Boolean theorems?

☒ Perfect induction: try all the finite number of possibilities.

☐ Using the Method of Frobenius

☒ By applying axioms and other theorems

☐ Theorems can't be proven; they just have to be accepted as true



Submit

Try again (1 attempt remaining)

Show answer

Consider the following truth table:

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

Sum of Products

1/1 point (graded)

Write a sum of products equation corresponding to the truth table above

☒ $Y = (\sim A)(\sim B) + A(\sim B)$

☐ $Y = (\sim A)(\sim B) + B$

☐ $Y = A \cdot B$



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Simplifying

1/1 point (graded)

Apply Boolean Algebra to your equation above to find a minimal sum-of-products equation

☐ $Y = (\sim A)(\sim B) + A(\sim B)$

☐ $Y = (\sim A + A)(\sim B)$

☐ $Y = \sim A$

☐ $Y = A$

☒ $Y = \sim B$



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Consider the following truth table. Note that we could write it in short hand as 00001110 by just considering the output column, ordered with the first row in the least significant bit.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Sum of Products

1/1 point (graded)

Write a sum of products expression from the truth table:

☒ $Y = (\sim A)(\sim B)C + (\sim A)B(\sim C) + (\sim A)BC$

☐ $Y = (\sim A)(B+C)$

☐ $Y = \sim(A)(\sim((\sim B)(\sim C)))$



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Simplification

1/1 point (graded)

Apply Boolean Algebra to find a minimal sum of products equation.

☐ $Y = (\sim A)(B+C)$

☒ $Y = (\sim A)(B) + (\sim A)C$

☐ $Y = (\sim A)(\sim B)C + (\sim A)B(\sim C) + (\sim A)BC$



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Logic to Gates

1/1 point (graded)

[Keyboard Help](#)

Drag the Boolean equations to the corresponding schematics.

A

$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC$$

A

$$Y = \overline{A}BC + A\overline{B}\overline{C} + \overline{A}BC$$

Reset

FEEDBACK


Good work! You can relate equations and schematics.

DeMorgan's Law

1/1 point (graded)

Simplify $Y = \sim((\sim A)(B+C))$ to sum-of-products form:☐ $(\sim A)B + (\sim A)C$ ☐ $A(\sim B)(\sim C)$ ☒ $A + (\sim B)(\sim C)$ ☐ $(\sim A)BC$ ☐ $\sim(A + (\sim B) + (\sim C))$ [Submit](#)[Try again \(1 attempt remaining\)](#) [Show answer](#)

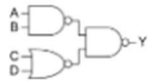Use bubble pushing to determine the function performed by the following circuit:



Multiple Choice

1/1 point (graded)

Boolean equation for circuit above:

☐ $Y = ABCD$ ☐ $Y = (A+B)CD$ ☐ $Y = AB(\sim C)(\sim D)$ ☒ $Y = AB + C + D$ ☐ $Y = AB(C+D)$ [Submit](#)[Try again \(1 attempt remaining\)](#) [Show answer](#)

X

1/1 point (graded)

In digital design, an X may mean (check all that apply):

☐ floating value

☒ uninitialized value

☒ contention

☒ don't care



Submit

Try again (1 attempt remaining)

Show answer

Z

1/1 point (graded)

In digital design, an Z may mean (check all that apply):

☒ floating value

☐ uninitialized value

☐ contention

☐ don't care



Submit

Try again (1 attempt remaining)

Show answer

Truth Tables and Karnaugh Maps

1/1 point (graded)

[Keyboard Help](#)

PROBLEM

Drag the truth tables to their corresponding Karnaugh Maps.

		AB	00	01	11	10
Y	C	0	1	1	1	0
	1	1	1	0	1	

		AB	00	01	11	10
Y	C	0	1	0	0	1
	1	1	1	0	1	

Reset

FEEDBACK

i Good work! You can relate truth tables and Karnaugh maps.

Karnaugh Maps and Boolean Equations

1/1 point (graded)

[Keyboard Help](#)

Drag the minimal sum-of-products equations to its corresponding Karnaugh map.

		AB	00	01	11	10
Y	C	0	1	1	1	0
	1	1	1	0	1	

		AB	00	01	11	10
Y	C	0	1	0	0	1
	1	1	1	0	1	

Reset

Consider the following Karnaugh map:

Y C	AB	00	01	11	10
		0	1	x	1
		0	1	x	0
		1	1	x	x

Minimal SOP Expression

1/1 point (graded)

Determine a minimal sum-of-products expression from the K-map.

☐ $Y = (\sim A)(\sim B)(\sim C) + (\sim A)(\sim B)C + AB(\sim C)$

☐ $Y = (\sim A)(\sim B) + AB(\sim C) + A(\sim B)C$

☐ $Y = (\sim A)(\sim B) + AB(\sim C)$

☐ $Y = (\sim A) + AB(\sim C)$

☐ $Y = (\sim A) + B(\sim C) + (\sim B)C$

☒ $Y = (\sim A) + B(\sim C)$



Submit

Try again (1 attempt remaining) ?

Show answer

Consider the following Karnaugh map:

Y CD	AB	00	01	11	10
		00	1	0	1
		01	1	x	x
		11	1	0	0
		10	1	1	0

Minimal SOP Expression

1/1 point (graded)

Determine a minimal sum-of-products expression from the K-map.

☐ $Y = (\sim A)(\sim B) + (\sim A)C(\sim D) + A(\sim C)(\sim D)$

☐ $Y = (\sim A)(\sim B) + (\sim B)(\sim D) + A(\sim C)$

☒ $Y = (\sim A)(\sim B) + (\sim A)C(\sim D) + A(\sim C)$

Consider the following circuit:



Multiple Choice

1/1 point (graded)

If $S = 1$, what is Y in the circuit above?

☒ 0

☐ 1

☐ X

☐ Z

☐ Not enough information to say



Submit

Try again (1 attempt remaining)

Show answer

Multiple Choice

1/1 point (graded)

The mux circuit above is equivalent to the following logic function:

☒ $Y = \sim S$

☐ $Y = 0$

☐ $Y = 1$

☐ $Y = (\sim S)D0 + SD1$




Submit

Try again (1 attempt remaining)

Show answer

Consider the following 4:1 multiplexer.

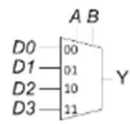

Multiple Choice

1/1 point (graded)

What values could you provide to {D3, D2, D1, D0} to make this mux compute $Y = A \text{ NAND } B$?

☐ {0, 0, 0, 0}

☒ {0, 1, 1, 1}

☐ {1, 1, 1, 0}

☐ {0, 0, 0, 1}

☐ {1, 0, 0, 0}



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Lecture Practice due Apr 8, 2023 10:37 PDT Completed

Numerical Input

1/1 point (graded)

Consider a decoder taking a 7-bit address input. How many outputs does it produce?

128



128

Submit


Try again (1 attempt remaining) ⓘ

Show answer

Consider the following component delays

Cell	Propagation Delay (ps)	Contamination Delay (ps)
NOT	6	4
NAND2	8	6
NOR2	10	8
NAND3	10	8
NOR3	12	10

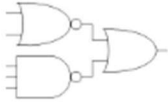and the circuit below. The OR gate is composed of a NOR followed by an inverter.



Propagation Delay

1/1 point (graded)

What is the propagation delay of this circuit (in ps)?



Submit

Try again (1 attempt remaining) ?

Show answer

Contamination Delay

1/1 point (graded)

What is the contamination delay of this circuit (in ps)?



Submit

Try again (1 attempt remaining) ?

Show answer