 


Consider the following clock divider built from a [74HC74 D flip-flop](#) and a [74HC04 inverter](#) (data sheets linked here). The divider receives a clock on the CLK terminal and produces an output on the Q terminal. The pin numbers are annotated on the schematic.

Suppose that the system operates under typical conditions (TYP column of the datasheet) at room temperature (25 C) with VCC = 4.5 V.



Propagation Delay

1/1 point (graded)

What is the propagation delay of the NOT gate (in ns)?



9

Submit

You have used 1 of 2 attempts

Save

Show answer

Setup Time

1/1 point (graded)

What is the setup time of the flip-flop with respect to the input (in ns)?



20

Submit

You have used 1 of 2 attempts

Save

Show answer

Clock-to-Q Delay

1/1 point (graded)

What is the clock-to-Q delay of the flip-flop (in ns)?



Submit

You have used 1 of 2 attempts

Save

Show answer

Clock Period

1/1 point (graded)

What is the minimum clock period for which the system will operate properly, assuming no clock skew (in ns)?



Submit

You have used 1 of 2 attempts

Save

Show answer

Output Behavior

1/1 point (graded)

Suppose CLK switches at 10 MHz. What frequency would Q switch at? Express your answer in MHz.



Submit

You have used 1 of 2 attempts

Save

Show answer

Dynamic Power

2.0/2.0 points (graded)

The Cpd entry on the data sheet represents the effective capacitance of the component for the purpose of dynamic power consumption calculations. Disregard input capacitance (C_i) for power calculations. The effective frequency of the flip-flop is the clock frequency (10 MHz), and the effective frequency of the inverter is the switching frequency of its input. Suppose that the system is on a breadboard that has an additional 10 pF of capacitance switching at the same frequency as Q. Use $V_{CC} = 5$ V. Compute the dynamic power consumption. Express your answer in μ W.



Submit

You have used 1 of 2 attempts

Save

Show answer

Static Power

1/1 point (graded)

Compute the static power drawn by the power supply pins. Ignore input leakage. Use $V_{CC} = 5$ V. The supply current is only specified at a higher V_{CC} , so conservatively use that figure. Express your answer in units of μ W.




Submit

You have used 1 of 2 attempts

Save

Show answer

 Consider the following two-dimensional plot of voltage-transfer characteristics. The yellow area are square, and the blue areas are symmetric. It's impossible to read this plot with complete precision, so the question will accept a reasonable range of answers.



Logic Function

2.0/2.0 points (graded)

What is the logic function performed by this system?

☐ NOT

☐ AND

☐ OR

☐ NAND

☐ NOR

☐ XOR

☒ XNOR



Submit

You have used 1 of 2 attempts

Save

Show answer

VIL

1/1 point (graded)

What is V_{IL} ?



Submit

You have used 1 of 2 attempts

Save

Show answer

VIH

1/1 point (graded)

What is V_{IH} ?



Submit

You have used 1 of 2 attempts

Save

Show answer

VOL

1/1 point (graded)

What is V_{OL} ?



Submit

You have used 2 of 2 attempts

Show answer

VOH

1/1 point (graded)

What is V_{OH} ?



Submit

You have used 1 of 2 attempts

Save

Show answer

Noise Margin

1/1 point (graded)

What is the smaller of the two noise margins?




Submit

You have used 1 of 2 attempts

Save

Show answer

Figure 5.20 from the textbook, repeated below, is a 4×4 unsigned multiplier that takes in two 4-bit inputs $A[3:0]$ and $B[3:0]$ and produces an 8-bit product $P[7:0]$.

 

The multiplier contains 12 full adder cells. Suppose the cells are implemented as shown below.

```
module fulladder(input  logic a, b, cin,
                 output logic s, cout);

    logic n1, n2, n3, x1;

    // sum
    xor gx1(x1, a, b);
    xor gx2(s, x1, cin);

    // carry
    and ga1(n1, a, b);
    and ga2(n2, a, cin);
    and ga3(n3, b, cin);
    or  go1(cout, n1, n2, n3);
endmodule
```

Suppose the cells have properties given in the following table

Cell	t_{pd} (ps)	t_{cd} (ps)	Relative Size
NOT	6	4	2
AND2	14	10	5
AND3	18	14	6
OR2	16	12	5
OR3	20	16	6
XOR2	24	18	9
NAND2	8	6	3
NAND3	12	10	4
NOR2	10	8	3
NOR3	14	12	4

Multiplication

1/1 point (graded)

Suppose $A[3:0] = 1010$ and $B[3:0] = 1110$. Express $P[7:0]$ in hexadecimal.



Submit

You have used 1 of 2 attempts

Save

Show answer

Circuit Cost

1/1 point (graded)

Determine the cost of the circuit, measured in the same units as the relative sizes.



548


Submit

You have used 1 of 2 attempts

Save

Show answer

 Consider the following possible critical paths annotated on the multiplier:



Critical Path

2.0/2.0 points (graded)

What is the longest path through the multiplier? (Descriptions are added in case you have trouble seeing color.)

- ☐ red (from the first column to P7)
- ☐ blue (from the first column to P6)
- ☒ purple (from the first column down the P4 column to P7)
- ☐ green (down the P3 column to P7)



Submit

You have used 1 of 2 attempts

Save

Show answer

Critical Path Cells

1/1 point (graded)

What are the elements on the critical path?

☐ $5AND2 + 4OR3 + 4XOR$

☐ $6AND2 + 5OR3 + 3XOR$

☐ $7AND2 + 6OR3 + 2XOR$

☒ $7AND2 + 6OR3 + 3XOR$



Submit

You have used 1 of 2 attempts

Save

Show answer

Propagation Delay

1/1 point (graded)

What is the propagation delay of the multiplier? Express your answer in ps.

290



290

Submit

You have used 1 of 2 attempts

Save

Show answer

Contamination Delay

1/1 point (graded)

What is the contamination delay of the multiplier? Express your answer in ps.

10



10


Submit

You have used 1 of 2 attempts

Save

Show answer

Consider the following circuit:

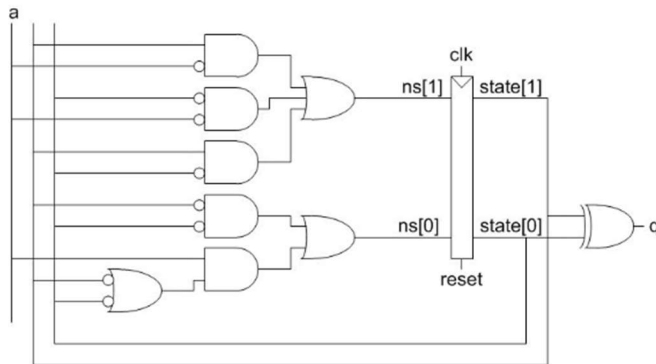

Download a SystemVerilog template and test vectors for this circuit.

fsm.sv

fsm.tv

The expected test vector outputs are given as x. You may change them for testing purposes, but may not change the inputs because that would mess up your hash.

Modify fsm.sv to describe the circuit with behavioral (not structural) SystemVerilog. Simulate and debug, and report the hash you obtained.

This MOOC cannot give partial credit, so the stakes for getting it right are high. Use the verification techniques you have learned in this class to confirm that your design is right.

Behavioral FSM

1/1 point (graded)

Check all the boxes below that apply to your behavioral FSM description:

☒ fsm has an always_ff block describing the state register

☐ fsm instantiates two flopr modules describing the state register

☒ the state register has a reset input

☐ the state register doesn't need reset because its state naturally starts at 0 when first turned on.

☐ fsm instantiates AND, OR, and NOT gates to structurally describe the circuit

☐ fsm uses assign statements with Boolean equations to describe the next state logic

☒ fsm uses a case statement to describe the next state logic



Submit

You have used 1 of 2 attempts

Save

Show answer

Hash

4.0/4.0 points (graded)

What hash did your testbench produce? Enter the hash as a 2-digit hexadecimal number with lowercase letters where applicable.

30



Submit

You have used 1 of 2 attempts

Save

Show answer