

## ❖ Lab 1 : Breadboarding Circuits

Lab due May 13, 2023 10:37 PDT Completed

Design a *full adder*. The inputs are  $A$ ,  $B$ , and  $C_{in}$ . The outputs are  $S$  and  $C_{out}$ . The full adder computes  $\{C_{out}, S\} = A + B + C_{in}$ . In other words, it sums the three inputs to produce a two-bit result, with  $S$  being the least significant bit and  $C_{out}$  being the most significant bit.  $C_{in}$  and  $C_{out}$  are called the carries. For example, if  $A = 1$ ,  $B = 0$ , and  $C_{in} = 1$ , the result is  $1 + 0 + 1 = 2_{10} = 10_2$ . Thus, the sum is 0 and the carry out is 1. Although the logic for a full adder is in the textbook and many other places, please work it out yourself from first principles.

### Full Adder Truth Table

1/1 point (graded)

 [Keyboard Help](#)

Drag 0s and 1s to complete a truth table for the full adder.

| Inputs   |     |     | Outputs   |     |
|----------|-----|-----|-----------|-----|
| $C_{in}$ | $B$ | $A$ | $C_{out}$ | $S$ |
| 0        | 0   | 0   | 0         | 0   |
| 0        | 0   | 1   | 0         | 1   |
| 0        | 1   | 0   | 0         | 1   |
| 0        | 1   | 1   | 1         | 0   |
| 1        | 0   | 0   | 0         | 1   |
| 1        | 0   | 1   | 1         | 0   |
| 1        | 1   | 0   | 1         | 0   |
| 1        | 1   | 1   | 1         | 1   |

 Reset