


❖ Problem Set 4: Timing, SystemVerilog

Problem Set due May 6, 2023 10:37 PDT Completed

Consider the following component delays

Cell	Propagation Delay (ps)	Contamination Delay (ps)	Setup Time (ps)	Hold Time (ps)
NOT	6	4		
NAND (2-input)	8	6		
NOR (2-input)	10	8		
NAND (3-input)	10	8		
NOR (3-input)	12	10		
Flop	20	15	10	5

 and the circuit below, in which registers are added to the circuit you analyzed in Problem Set 3.



Cycle Time

1/1 point (graded)

What is the minimum clock cycle time of this circuit, in the absence of clock skew? Express your answer in picoseconds.



72

Submit

Try again (1 attempt remaining) ⓘ

Show answer

Clock Frequency

1/1 point (graded)

What is the maximum clock frequency? Express your answer in GHz.



Submit

Try again (1 attempt remaining)

Show answer

Hold Time

1/1 point (graded)

How much clock skew could this circuit endure before possibly violating the hold time? Express your answer in picoseconds.



Problem Set due May 6, 2023 10:37 PDT Completed

Synchronizers

1/1 point (graded)

A synchronizer is built from a pair of flip-flops. The flip-flops have a setup time of 50 ps, T_0 of 20 ps, and τ of 30 ps. The synchronizer samples an asynchronous input that changes 100 million times per second. What is the minimum clock period of the synchronizer to achieve a mean time between failures (MTBF) of 100 years? Express your answer in ns.



Submit

Try again (1 attempt remaining)

Show answer

Consider the following possible SystemVerilog descriptions of a 2:4 Decoder.

```
module dec2to4a(input  logic [1:0] a,
               output logic [3:0] y);

    assign y[3] = a[1] & a[0];
    assign y[2] = a[1] & ~a[0];
    assign y[1] = ~a[1] & a[0];
    assign y[0] = ~a[1] & ~a[0];
endmodule
```

```
module dec2to4b(input  logic [1:0] a,
               output logic [3:0] y);

    logic [1:0] ab;

    not gn1(ab[1], a[1]);
    not gn0(ab[0], a[0]);
    and ga3(y[3], a[1], a[0]);
    and ga2(y[2], a[1], ab[0]);
    and ga1(y[1], ab[1], a[0]);
    and ga0(y[0], ab[1], ab[0]);
endmodule
```

```
module dec2to4c(input  logic [1:0] a,
               output logic [3:0] y);

    always_comb
    case(a)
        2'b00: y = 4'b0001;
        2'b01: y = 4'b0010;
        2'b10: y = 4'b0100;
        2'b11: y = 4'b1000;
    endcase
endmodule
```

```
module dec2to4d(input  logic [1:0] a,
               output logic [3:0] y);

    always_comb
    begin
        y = 4'b0;
        y[a] = 1;
    end
endmodule
```

```
module dec2to4e(input  logic [1:0] a,
               output logic [3:0] y);

    always_comb
    if      (a == 2'b00) y = 4'b0001;
    else if (a == 2'b01) y = 4'b0010;
    else if (a == 2'b10) y = 4'b0100;
    else      y = 4'b1000;
endmodule
```

Correctness

1/1 point (graded)

Which of these descriptions are logically correct? Check all that apply.

☒ dec2to4a

☒ dec2to4b

☒ dec2to4c

☒ dec2to4d

☒ dec2to4e



Submit

Try again (1 attempt remaining) ⓘ

Show answer

Style

1/1 point (graded)

Which of the descriptions above would be the best idiom for a 2:4 decoder?

☐ (a) because it is easiest to understand the function of a block from its Boolean equations

☐ (b) because structural Verilog is more readable than behavioral Verilog

☒ (c) or (d) because it is easiest to understand the function of a block from its truth table in (c), while (d) is concise and scales well to larger decoders

☐ (e) because expressing a truth table with if statements is clearer and more concise than using case statements






Submit

Try again (1 attempt remaining) ⓘ

Show answer

Consider the following SystemVerilog module and possible implementations.
   
```
module exercise(input logic [3:1] a,  
               output logic [1:0] y);  
  
    always_comb  
        if      (a[3]) y = 2'b11;  
        else if (a[2]) y = 2'b10;  
        else if (a[1]) y = 2'b01;  
        else      y = 2'b00;  
  
endmodule
```



HDL Synthesis

1/1 point (graded)

Which hardware schematic is implied by the code above? Simplify as much as possible.

☐ (a)

☒ (b)

☐ (c)

☐ none of the above



Submit

Try again (1 attempt remaining) ⓘ

Show answer

HDL Idioms

1/1 point (graded)

Which is the name of the building block implied by the "exercise" module above?

☐ Decoder

☐ Multiplexer

☒ Priority Encoder

☐ Gray Code Counter

☐ Level to Pulse Converter

☐ Finite State Machine



Submit

Try again (1 attempt remaining) ⓘ

Show answer